

# Lecture 7: Fourier Series (3/3)

Dr Gavin M Abernethy

Further Mathematics, Signals and Systems

Today we shall cover:

- Applying Fourier Series to circuit analysis.
- In particular, if we are given an **input signal** and the system's **transfer function**:
  1. We can determine the **Fourier series of the input**.
  2. Then (easily!) calculate the **Fourier series of the output**.

We shall be using the complex form of Fourier Series.

# Complex Fourier Series

## Complex form of the Fourier Series:

$$f(t) = \frac{a_0}{2} + \operatorname{Re} \left\{ \sum_{n=1}^{\infty} A_n e^{jn\omega t} \right\}$$


The complex Fourier coefficients (“phasors”) are obtained by Laplace transforms:

## Phasor of the $n^{\text{th}}$ harmonic:

$$A_n = \frac{2}{T} \bar{g}(jn\omega)$$
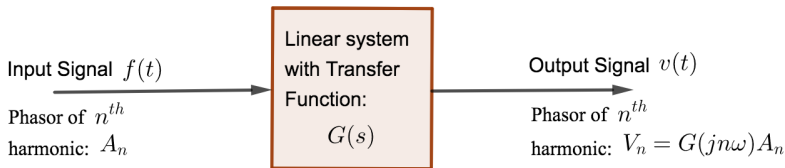
# Concept: Use of Fourier Series in Circuit analysis

- Let  $f(t)$  be a periodic input to a linear system.
- What is the effect of the system on the input, encoded in its transfer function  $G(s)$ ?
- The  $n^{th}$  harmonic is modified by the **frequency response function**  $G(jn\omega)$ .



# Concept: Use of Fourier Series in Circuit analysis

Let  $A_n$  be the phasor for the  $n^{th}$  harmonic of the input.  
Then the output phasor  $V_n$  is given by:

Phasor of the  $n^{th}$  harmonic of the output:

$$V_n = G(jn\omega)A_n$$

So the Fourier Series of the output  $v(t)$  is:

Complex Fourier Series of output signal:

$$v(t) = G(0)\frac{a_0}{2} + \operatorname{Re}\left\{ \sum_{n=1}^{\infty} G(jn\omega)A_n e^{jn\omega t} \right\}$$

This is one reason why Fourier Series (esp. complex form) is useful.

- Input phasors are modified by the frequency response function to produce the corresponding output phasor.
- The modulus of  $A_n$  is multiplied by the modulus of  $G(jn\omega)$  to give the amplitude of the  $n^{th}$  harmonic of the output.
- The phase angle (the argument) of  $G(jn\omega)$  is added to the phase angle of  $A_n$  to give the phase angle of the  $n^{th}$  harmonic  $V_n$  of the output.

# Distortion

## Amplitude Distortion

If the modulus of  $G(jn\omega)$  depends on  $n$ , the amplitude of each harmonic may be scaled by a different factor.

## Phase Distortion

If the phase angle of  $G(jn\omega)$  depends on  $n$ , each phase angle may be altered by a different amount.

Often both types of distortion occur. Either will result in the output waveform having a different shape to the input waveform.

# Method: Determining Fourier Series of an output signal


Given a linear circuit and an input signal  $f(t)$ , we wish to determine the output signal  $v(t)$ :

- 1 Determine the transfer function  $G(s)$  of the system.
- 2 Using the method of Laplace transforms, determine the complex Fourier Series of input  $f(t)$ .
- 3 Evaluate the transfer function at  $s = 0$  to find  $G(0)$ .
- 4 Multiply the DC level of  $f(t)$  by  $G(0)$  to determine the DC level of the output.
- 5 Multiply the phasors  $A_n$  of the input by the frequency response function  $G(jn\omega)$  to determine the phasors of the output.
- 6 Write down the complex Fourier Series of output  $v(t)$ .



# Example 1

Consider the circuit shown.

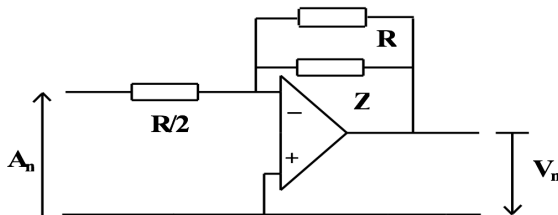

The transfer function for this system is:

$$G(s) = 2 \left( \frac{1 + sCR}{1 + 2sCR} \right)$$

# Example 1

The frequency response function is therefore:

$$G(jn\omega) = 2 \left( \frac{1 + jn\omega CR}{1 + 2jn\omega CR} \right)$$

and at  $s = 0$ :

$$G(0) = 2 \left( \frac{1 + 0}{1 + 0} \right) = 2$$

Therefore, given a general input signal with Fourier series:

$$e(t) = \frac{a_0}{2} + \operatorname{Re} \left\{ \sum_{n=1}^{\infty} A_n e^{jn\omega t} \right\}$$

the output from this system will be:

$$v(t) = a_0 + \operatorname{Re} \left\{ 2 \sum_{n=1}^{\infty} \frac{1 + jn\omega CR}{1 + 2jn\omega CR} A_n e^{jn\omega t} \right\}.$$

# Example 1

For example, consider if the input signal was this pulse wave  $e(t)$ :



In this case the input phasor is:

$$A_n = a_n - jb_n = \frac{-jE}{\pi n} (1 - \cos(\pi n)) = \begin{cases} \frac{-2Ej}{\pi n} & \text{for odd } n, \\ 0 & \text{for even } n, \end{cases}$$

and input DC level:  $\frac{a_0}{2} = \frac{E}{2}$

## Example 1

Hence for this specific input, the output phasor is:

$$V_n = G(jn\omega)A_n = 2 \left( \frac{1 + jn\omega CR}{1 + 2jn\omega CR} \right) \times \begin{cases} \frac{-2Ej}{\pi n} & \text{for odd } n, \\ 0 & \text{for even } n, \end{cases}$$

The output DC level is:

$$G(0) \times \frac{a_0}{2} = 2 \times \frac{E}{2} = E$$

So the Fourier Series of the output signal is:

$$v(t) = E + \operatorname{Re} \left\{ \frac{-4Ej}{\pi} \sum_{\text{odd } n \in \mathbb{N}} \frac{(1 + jn\omega CR)}{n(1 + 2jn\omega CR)} e^{jn\omega t} \right\}, \quad \omega = \frac{2\pi}{T}$$


# Linear Circuit Analysis using Fourier Series

This process consolidates much of what we have studied on this module:

- Finding and manipulating the **transfer function** of a system (you **must** be able to do this!)
- Using Laplace transforms to find the **complex Fourier Series** of an input signal.
- Combining these to determine the Fourier Series of the **output signal**.

## Example 2 - Practice

Consider this circuit:

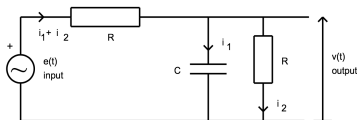

$$e(t) = R(i_1(t) + i_2(t)) + Ri_2(t)$$

$$\frac{1}{C} \int_0^t i_1(t) dt = Ri_2(t)$$

$$v(t) = Ri_2(t)$$

$R$  and  $C$  are positive constants,  $e(t)$  is the input signal and  $v(t)$  is the output signal. Given a general input,

$$e(t) = \frac{a_o}{2} + Re \left\{ \sum_{n=1}^{\infty} A_n e^{jn\omega t} \right\}$$

Determine the Fourier Series of the corresponding output  $v(t)$ .

## Example 2 - Practice

Taking Laplace transforms of each equation:

$$(1) \quad \bar{e}(s) = R(\bar{i}_1 + 2\bar{i}_2)$$

$$(2) \quad \frac{1}{sC}\bar{i}_1 = R\bar{i}_2$$

$$(3) \quad \bar{v}(s) = R\bar{i}_2$$

Then to find the transfer function...

1. Rearrange (2), then substitute it into (1) to eliminate  $\bar{i}_1$ :

$$\text{From (2): } \bar{i}_1 = sCR\bar{i}_2$$

$$\begin{aligned}\therefore \bar{e}(s) &= R(\bar{i}_1 + 2\bar{i}_2) = R(sCR\bar{i}_2 + 2\bar{i}_2) \\ &= R\bar{i}_2(sCR + 2)\end{aligned}$$

## Example 2 - Practice

2. Substitute in (3) to eliminate  $\bar{i}_2$ :

$$\bar{e}(s) = \bar{v}(s)(sCR + 2)$$

Finally, rearrange this to the transfer function:

$$G(s) = \frac{\bar{v}(s)}{\bar{e}(s)} = \frac{1}{sCR + 2}$$

∴ Frequency response function:

$$G(jn\omega) = \frac{1}{jn\omega CR + 2}.$$



## Example 2 - Practice

Let  $A_n$  be the phasors of the  $n^{th}$  harmonics of the input with angular frequency  $n\omega$ .

Then the phasor of the  $n^{th}$  harmonic of the output is:

$$V_n = G(jn\omega)A_n = \left( \frac{1}{2 + jn\omega CR} \right) A_n$$

The DC level of the output is:

$$\frac{V_0}{2} = G(0) \times \frac{1}{2} a_0 = \left( \frac{1}{2 + 0 \cdot CR} \right) \times \frac{1}{2} a_0 = \frac{1}{4} a_0$$

## Example 2 - Practice

Hence if the Fourier series of the input signal is

$$e(t) = \frac{a_0}{2} + \operatorname{Re} \left\{ \sum_{n=1}^{\infty} A_n e^{jn\omega t} \right\}$$

then the output will be:


$$\begin{aligned} v(t) &= G(0) \frac{1}{2} a_0 + \operatorname{Re} \left\{ \sum_{n=1}^{\infty} G(jn\omega) A_n e^{jn\omega t} \right\} \\ &= \frac{a_0}{4} + \operatorname{Re} \left\{ \sum_{n=1}^{\infty} \frac{1}{2 + jn\omega CR} A_n e^{jn\omega t} \right\}, \quad \omega = \frac{2\pi}{T} \end{aligned}$$

$G(jn\omega)$  is complex and frequency dependent,

$\implies$  expect both amplitude and phase distortion.
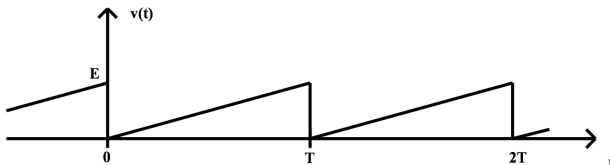
## Example 2 - Practice

Consider if the input was the sawtooth waveform:



Last week we saw that this has phasor:

$$A_n = \frac{Ej}{\pi n}$$

and DC level:

$$\frac{a_0}{2} = \frac{E}{2}$$

## Example 2 - Practice

Hence for this specific input, the output phasor is:

$$\begin{aligned} V_n &= G(jn\omega)A_n = \frac{1}{2 + jn\omega CR} \times \frac{Ej}{\pi n} \\ &= \frac{Ej(2 - jn\omega CR)}{\pi n(2 + jn\omega CR)(2 - jn\omega CR)} = \frac{E(2j + n\omega CR)}{\pi n(4 + n^2\omega^2 C^2 R^2)} \end{aligned}$$

The output DC level is:

$$G(0) \times \frac{a_0}{2} = \frac{1}{2} \times \frac{E}{2} = \frac{E}{4}$$

$\therefore$  Complex Fourier Series of the output signal:

$$v(t) = \frac{E}{4} + \operatorname{Re} \left\{ \sum_{n=1}^{\infty} \frac{E(2j + n\omega CR)}{\pi n(4 + n^2\omega^2 C^2 R^2)} e^{jn\omega t} \right\}, \quad \omega = \frac{2\pi}{T}$$

# Summary

After today, you should be able to ...

- (From last week) Determine the complex Fourier Series of an input signal from the waveform.
- (From week 4) Find the transfer function from the equations of a circuit.
- Determine the Fourier Series of the output signal of a circuit, given the input.

# This Week

This week's lecture corresponds to Section 3.8 of the Course Notes.

Before this week's tutorial:


- Attempt Tutorial sheet 7

In the following lecture we will move on to the final topic:

## **Matrix algebra**

# Extra Question

Consider the following circuit:

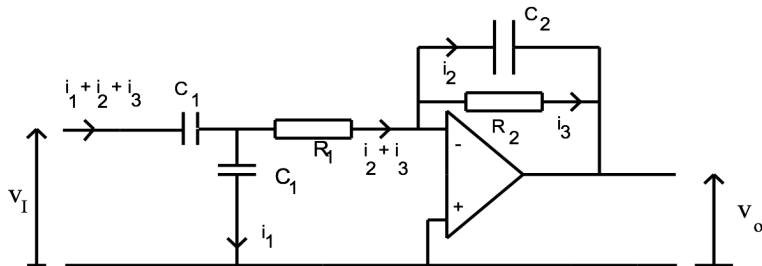

## Extra Question

These equations describe the currents  $i_1, i_2, i_3$ , input voltage  $v_i$  and output voltage  $v_o$ , where  $R_1, R_2, C_1, C_2$  are positive constants.

$$v_i(t) = \frac{1}{C_1} \int_0^t (i_1(t) + i_2(t) + i_3(t)) dt + R_1 (i_2(t) + i_3(t))$$

$$\frac{1}{C_1} \int_0^t i_1(t) dt = R_1 (i_2(t) + i_3(t))$$

$$R_2 i_3(t) = \frac{1}{C_2} \int_0^t i_2(t) dt$$

$$v_o(t) = -R_2 i_3(t)$$

For a general input  $v_i(t)$ , find the Fourier Series of the output  $v_o(t)$



## Extra Question

The transfer function is:

$$G(s) = \frac{\bar{v}_o}{\bar{v}_i} = \frac{-sC_1R_2}{(1 + 2sC_1R_1)(1 + sC_2R_2)}.$$

Therefore, if the Fourier series for the input wave is:

$$v_i(t) = \frac{a_0}{2} + \operatorname{Re}\left\{ \sum_{n=1}^{\infty} A_n e^{jn\omega t} \right\}, \quad \omega = \frac{2\pi}{T},$$

then the corresponding Fourier series for the output is:

$$\begin{aligned} v_o(t) &= \frac{a_0}{2} G(0) + \operatorname{Re}\left\{ \sum_{n=1}^{\infty} G(jn\omega) A_n e^{jn\omega t} \right\} \\ &= \operatorname{Re}\left\{ \sum_{n=1}^{\infty} \frac{-jn\omega C_1 R_2}{(1 + 2jn\omega C_1 R_1)(1 + jn\omega C_2 R_2)} A_n e^{jn\omega t} \right\} \end{aligned}$$